

UNIT III

Number System and Logic Gates

1. A binary digit is called a _____

- a. Bit
- b. Byte
- c. Number
- d. Character

Ans: a

2. A byte corresponds to.

- a. 4 bits
- b. 8 bits
- c. 16 bits
- d. 32 bits

Ans: b

3. The 5 V level of a digital signal is called a logical 1 or HIGH

- a. True
- b. False

Ans: a

4. The +12V level of a digital signal is also called a logical-----

- a. 0 or LOW
- b. 0 or HIGH
- c. 1 or LOW
- d. 1 or HIGH

Ans: d

5. Positive logic in logic circuit is one in which

- a. Logic 0 and 1 are represented by 0 and positive voltages respectively.
- b. Logic 0 and 1 are represented by negative and positive voltages respectively.
- c. Logic 0 voltage level is higher than logic 1 voltage level.

d. Logic 0 voltage level is lower than logic 1 voltage level.

Ans: d

6. The Boolean expression $Y=(AB)'$ is logically equivalent to what single gate?

- a. NAND
- b. NOR
- c. AND
- d. OR

Ans: a

7. The NAND gate output will be low if the two inputs are

- a. 00
- b. 01
- c. 10
- d. 11

Ans: d

8. The output of a logic gate is 1 when all its inputs are at logic 0. The gate is either

- a. a NAND or an EX-OR
- b. an OR or an EX-NOR
- c. an AND or an EX-OR
- d. a NOR or an EX-NOR

Ans: d

9. The NOR gate output will be high if the two inputs are

- a. 00
- b. 01
- c. 10
- d. 11

Ans: a

10. When an input signal A=11001 is applied to a NOT gate serially, its output signal is

- a. 00111
- b. 00110
- c. 10101
- d. 11001

Ans: b

11. How many NAND circuits are contained in a 7400 NAND IC?

- a. 1
- b. 2
- c. 4
- d. 8

Ans: c

12. The AND gates give high output when both inputs are ?

- a. high, high
- b. high, low
- c. low, high
- d. low,low

Ans: a

13. The OR gates give low output when both inputs are ?

- a. high, high
- b. high, low
- c. low, low
- d. low,high

Ans: c

14. The logic gate that will have HIGH or "1" at its output when any one of its inputs is HIGH is an:

- a. OR gate
- b. AND gate

c. NOR gate

d. NOT gate

Ans: a

15. Exclusive-OR (XOR) logic gate can be constructed from what logic gates?

- a. OR gates only
- b. AND gates and NOT gates
- c. AND gates, OR gates, and NOT gates
- d. OR gates and NOT gates

Ans: c

16. A NAND gate has:

- a. LOW inputs and a LOW output
- b. HIGH inputs and a HIGH output
- c. LOW inputs and a HIGH output
- d. None of the these

Ans: c

17. The basic logic gate whose output is the complement of the input is the:

- a. OR gate
- b. AND gate
- c. INVERTER gate
- d. Comparator

Ans: c

18. What input values will cause an AND logic gate to produce a HIGH output?

- a. At least one input is HIGH.
- b. At least one input is LOW.
- c. All inputs are HIGH.
- d. All inputs are LOW.

Ans: c

19. The NAND gates give low output when both inputs are.... ?

- a. low, high
- b. high, low
- c. high, high
- d. low, low

Ans: c

20. A XOR gate has inputs A and B and output Y. Then the output equation is

- a. $Y = A + B$
- b. $Y = AB + A'B$
- c. $AB + AB'$
- d. $AB' + A'B$

Ans: d

21. In a 3 input NAND gate, the number of states in which output is 1 equals

- a. 1
- b. 2
- c. 3
- d. 4

Ans: a

22. In a 3 input NOR gate, the number of states in which output is 1 equals

- a. 1
- b. 2
- c. 3
- d. 4

Ans: a

23. An AND gate has three inputs A,B,C out of total 8 input states, output is 1 in

- a. 1 states
- b. 2 states
- c. 3 states
- d. 4 states

Ans: a

24. An NOR gate has two inputs A and B, output is 1 if

- a. $A = 0, B = 0$
- b. $A = 1, B = 0$
- c. $A = 0, B = 1$
- d. $A = 1, B = 1$

Ans: a

25. The total number of input states for 4 input OR gate is

- a. 20
- b. 16
- c. 12
- d. 8

Ans: b

26. The gate whose output is LOW if and only if all inputs are HIGH, is

- a. NAND
- b. NOR
- c. OR
- d. AND

Ans: a

27. A waveform that has just two distinct voltages, such as 0 V and 12 V, is called as ----- signal.

- a. AM
- b. Analog
- c. FM
- d. Digital

Ans: d

28. The positive logic circuit is one in which
a. Logic 0 and 1 are represented by 0 and positive voltages respectively

- b. Logic 0 and 1 are represented by negative and positive voltages respectively
- c. Logic 0 voltage level is higher than logic 1 voltage level
- d. Logic 0 voltage level is lower than logic 1 voltage level

Ans: d

29. IC s are
- a. analog
 - b. digital
 - c. both analog and digital
 - d. mostly analog

Ans: c

30. A NOT gate has...
- a. Two inputs and one output
 - b. One input and one output
 - c. One input and two outputs
 - d. none of above

Ans: b

31. In a 4 input OR gate, the total number of High outputs for the 16 input states are
- a. 16
 - b. 15
 - c. 13
 - d. none of above

Ans: b

32. The 74LS08 chip contains----- gates.
- a. 4
 - b. 5
 - c. 6
 - d. 8

Ans: a

33. A 14 pin AND gate IC has ----- AND gates
- a. 8
 - b. 6
 - c. 4
 - d. 2

Ans: c

34. A 14 pin NOT gate IC has----- NOT gates
- a. 8
 - b. 6
 - c. 4
 - d. 2

Ans: b

35. Logically, the output of a NOR gate would have the same Boolean expression as an:
- a. NAND gate immediately followed by an INVERTER
 - b. OR gate immediately followed by an INVERTER
 - c. AND gate immediately followed by an INVERTER
 - d. NOR gate immediately followed by an INVERTER

Ans: b

36. Which of following are known as universal gates?
- a. NAND & NOR
 - b. AND & OR
 - c. XOR & OR
 - d. none

Ans: a

37. The number of bits in a nibble is.
- a. 16
 - b. 5
 - c. 4

d. 8

Ans: c

38. Which of the following binary numbers is equivalent to decimal 10.

- a. 1000
- b. 1100
- c. 1010
- d. 1001

Ans: c

39. Numbers are stored and transmitted inside a computer in.

- a. binary form
- b. ASCII code form
- c. decimal form
- d. alphanumeric form

Ans: a

40. Logic gates are the examples of_____.

- a. LSI
- b. MSI
- c. SSI
- d. any other

Ans: c

41. MUX is an example of_____.

- a. LSI
- b. MSI
- c. SSI
- d. any other

Ans: b

42. The term VLSI generally refers to a digital IC having

- a. more than 1000 gates
- b. more than 100 gates

c. more than 1000 but less than 9999 gates

d. more than 100 but less than 999 gates

Ans: a

43. The observation that a bubbled input OR gate is interchangeable with a bubbled output AND gate is referred to as:

- a. a Karnaugh map
- b. DeMorgan's second theorem
- c. the commutative law of addition
- d. the associative law of multiplication

Ans: b

44. What value of A, B, C, and D satisfy the following simultaneous Boolean equations?

$$\begin{aligned}A+AB &= 0, \\AB &= AC, \\AB+AC+CD &= CD.\end{aligned}$$

- a. $A = 0, B = 0, C = 0, D = 1$
- b. $A = 1, B = 1, C = 0, D = 0$
- c. $A = 1, B = 0, C = 1, D = 1$
- d. $A = 1, B = 0, C = 0, D = 0$

Ans: a

45. $AB+AB' =$

- a. B
- b. A
- c. 1
- d. 0

Ans: b

46. Boolean Algebra obeys

- a. commutative law
- b. associative law
- c. distributive law
- d. all of the above

Ans: d

47. The first contribution to logic was made by

- a. George Boole
- b. Copernicus
- c. Aristotle
- d. Shannon

Ans: a

48. One of DeMorgan's theorems states that $A'+B'=(A.B)'$. Simply stated, this means that logically there is no difference between:

- a. a NAND gate and an AND gate with a bubbled output
- b. a NOR gate and an AND gate with a bubbled output
- c. a NOR gate and a NAND gate with a bubbled output
- d. a NAND gate and an OR gate with a bubbled input

Ans: d

49. According to commutative law of addition:

- a. $AB = BA$
- b. $A = A + B$
- c. $A + B = B + A$
- d. $A + (B + C) = (A + B) + C$

Ans: c

50. Which of the examples below expresses the commutative law of multiplication?

- a. $A + B = B + A$
- b. $A \cdot B = B + A$
- c. $A \cdot (B \cdot C) = (A \cdot B) \cdot C$
- d. $A \cdot B = B \cdot A$

Ans: d

51. From following which Boolean Expression is not valid:

- a. $A \cdot 0 = A$
- b. $A \cdot 1 = A$
- c. $A \cdot 0 = 0$
- d. $A \cdot A = A$

Ans: a

52. Which of the following Boolean algebra rules is correct?

- a. $A.A' = 1$
- b. $A + AB = A + B$
- c. $A + A'B = A + B$
- d. $A.(A + B) = B$

Ans: c

53. Which of the examples below expresses the distributive law of Boolean algebra?

- a. $A \cdot (B \cdot C) = (A \cdot B) + C$
- b. $A + (B + C) = (A \cdot B) + (A \cdot C)$
- c. $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$
- d. $(A + B) + C = A + (B + C)$

Ans: c

54. When simplified with Boolean Algebra $(x + y) \cdot (x + z)$ simplifies to

- a. x
- b. $x + xy + z$
- c. $x + yz$
- d. $x + yz$

Ans: d

55. $A + A.B =$

- a. B
- b. A.B
- c. A
- d. A or B

Ans: c

56. $A \cdot 0 =$

- a. 1
- b. A
- c. 0
- d. A or 1

Ans: c

57. $(A + B) \cdot C =$

- a. $A \cdot B + C$
- b. $A \cdot B + A \cdot C$
- c. A
- d. $(A+B) \cdot (A+C)$

Ans: d

58. Which is correct?

- a. $A \cdot A = 0$
- b. $A + 1 = A$
- c. $A + A' = 1$
- d. $A' \cdot A' = 0$

Ans: c

59. The logical expression $Y = C + C'B$ is equivalent to

- a. $Y = C + B$
- b. $Y = CB$
- c. $Y = C' + B$
- d. $Y = C + B'$

Ans: a

60. The logical expression $Y = A + AB$ is equivalent to

- a. $Y = A + B$
- b. $Y = A$
- c. $Y = A' + B$
- d. $Y = A + B'$

Ans: b

61. Boolean expressions for the output of Ex-NOR logic gate with inputs A and B

- a. $AB' + A'B$
- b. $(AB)' + AB$
- c. $(A' + B) \cdot (A + B')$
- d. $(A' + B)' \cdot (A + B)$

Ans: c

62. The minimum number of OR gates required to implement $Y = A + AB' + AB'C$ is equal to

- a. 2
- b. 1
- c. 4
- d. 7

Ans: a

63. Given logical function of four variables $F(A, B, C, D) = (A + BC) \cdot (B + CD)$. The function as sum of product will be

- a. $AB + BC + ACD + BCD$
- b. $AB + AB + AC'D + BCD$
- c. $(AB + AB)' + ACD + BC'D$
- d. $AB' + A'B + A'CD + BCD$

Ans: a

64. How many AND gates are required to realize $Y = CD + EF + G$?

- a. 4
- b. 5
- c. 3
- d. 2

Ans: d

65. The expression $Y = AC + BD + EF$ is

- a. POS
- b. SOP

- c. hybrid
- d. none of above

Ans: b

66. The expression $Y = \sum m(0,1,3,4)$ is

- a. POS
- b. none of these
- c. hybrid
- d. SOP

Ans: d

67. In which function, is each term known as min term?

- a. POS
- b. SOP
- c. hybrid
- d. none of above

Ans: b

68. In the expression $A + BC$, the total number of min terms will be

- a. 2
- b. 3
- c. 4
- d. 5

Ans: a

69. The expression $Y = \prod M(0,1,3,4)$ is

- a. POS
- b. SOP
- c. hybrid
- d. none of above

Ans: a

70. Which of the following is true?

- a. SOP is a two level logic
- b. POS is a two level logic
- c. both SOP and POS are two level logic
- d. Hybrid function is two level logic

Ans: c

71. In which function, is each term known as max term?

- a. POS
- b. SOP
- c. hybrid
- d. none of above

Ans: a

72. What are the two types of basic adder circuits?

- a. half adder and full adder
- b. half adder and parallel adder
- c. asynchronous and synchronous
- d. one's complement and two's complement

Ans: a

73. The result of binary addition $1+1$ is

- a. 1
- b. 0
- c. 10
- d. 4

Ans: c

74. How many inputs does a Half-adder have?

- a. 1
- b. 2
- c. 3
- d. 4

Ans: b

75. How many outputs does a half adder have?

- a. 1
- b. 2
- c. 3
- d. 4

Ans: b

76. A full adder logic circuit will have

- a. Two inputs and one output
- b. Three inputs and three outputs
- c. Two inputs and two outputs
- d. Three inputs and two outputs

Ans: d

77. A combinational circuit that performs the addition of two input bits and a carry from the previous lower significant position is called

- a. Full-adder
- b. Half-adder
- c. Full-subtractor
- d. Half-subtractor

Ans: a

78. How many inputs will require for a 2:1 multiplexer?

- a. 5
- b. 8
- c. 2
- d. 1

Ans: c

79. The number of control lines for 2 to 1 multiplexer is

- a. 2
- b. 1
- c. 3
- d. 5

Ans: b

81. The number of control lines for a 8 – to – 1 multiplexer is

- a. 2
- b. 3

c. 4

d. 5

Ans: b

82. How many select lines will a 16 to 1 multiplexer will have?

- a. 4
- b. 3
- c. 5
- d. 1

Ans: a

83. How many outputs will require for a 1:4 demultiplexer?

- a. 4
- b. 8
- c. 2
- d. 1

Ans: a

84. The number of control lines i.e. select lines for 1 to 4 demultiplexer is

- a. 2
- b. 4
- c. 3
- d. 5

Ans: a

85. The number of control lines for 16 to 1 demultiplexer is

- a. 2
- b. 4
- c. 3
- d. 5

Ans: b

86. The number of control lines for 32 to 1 multiplexer is

- a. 4
- b. 5
- c. 16
- d. 6

Ans: b

87. One application of a digital multiplexer is to facilitate:

- a. code conversion
- b. parity checking
- c. parallel-to-serial data conversion
- d. data generation

Ans: c

88. What is applicable for demultiplexers ?

- a. decimal to hexadecimal
- b. single input, multiple outputs
- c. ac to dc
- d. odd parity to even parity

Ans: b

89. Output of combinational circuit depends upon

- a. Future input
- b. Present input
- c. Past and present
- d. None of these

Ans: b

90. Multiplexer is

- a. Combinational circuits
- b. sequential circuits
- c. either sequential or combinational circuits
- d. none of above

Ans: a

91. Which of the following circuits come under the class of combinational logic

circuits? 1. Full adder 2. Full subtractor 3. Half adder 4. J-K flip-flop 5. Counter

Select the correct answer from the codes given below:

- a. 1 only
- b. 3 and 4
- c. 4 and 5
- d. 1, 2 and 3

Ans: d

92. Which of the following circuits come under the class of sequential logic

circuits? 1. Full adder 2. Full subtractor 3. Half adder 4. J-K flip-flop 5. Counter

Select the correct answer from the codes given below:

- a. 1 and 2
- b. 2 and 3
- c. 3 and 4
- d. 4 and 5

Ans: d

93. Clock is a---- signal.

- a. rectangular
- b. triangular
- c. pulse
- d. Any other

Ans: a

94. A flip flop is a

- a. combinational circuit
- b. memory element
- c. arithmetic element
- d. memory or arithmetic

Ans: b

95. The basic storage element in a digital system is

- a. flip flop
- b. counter
- c. multiplexer
- d. encoder

Ans: a

96. ____FF is used to provide delay in circuit.

- a. SR
- b. D
- c. JK
- d. any other

Ans: b

97. In a D latch

- a. a high D sets the latch and low D resets it
- b. a low D sets the latch and high D resets it
- c. race can occur
- d. none of above

Ans: a

98. ____is basically group of FFs

- a. counter
- b. register
- c. latch
- d. Any other

Ans: b

99. The simplest register is

- a. buffer register
- b. shift register
- c. controlled buffer register
- d. bidirectional register

Ans: a

100. The basic shift register operations are

- a. serial in serial out
- b. serial in parallel out
- c. parallel in serial out
- d. all of above

Ans: d

101. SIPO stands for-----

- a. serial in parallel out
- b. serial in serial out
- c. serial
- d. Any other

Ans: a

102. A universal shift register can shift

- a. from right to left
- b. from left to right
- c. both from right to left and left to right
- d. none of above

Ans: c

103. An 8 bit binary number is to be entered into an 8 bit serial shift register. The number of clock pulses required is

- a. 1
- b. 2
- c. 4
- d. 8

Ans: d

104. An 8 bit binary number is to be entered into an 8 bit parallel-in shift register.

The number of clock pulses required is

- a. 1
- b. 2
- c. 4
- d. 8

Ans: a

105. The digital circuit used for counting pulse is known as_____.

- a. counter
- b. FF
- c. register
- d. any other

Ans: a

106. A counter is a

- a. Sequential ckt
- b. Combinational ckt
- c. both combinational and sequential ckt
- d. none of above

Ans: a

107. IC counters are

- a. synchronous only
- b. asynchronous only
- c. both synchronous and asynchronous
- d. none of above

Ans: c

108. A counter has 4 flip flops. The total number of states are

- a. 8
- b. 10
- c. 16
- d. 15

Ans: c

109. A counter has N flip flops. The total number of states is

- a. N
- b. 2N
- c. N²

d. 4N

Ans: b

110. A 3 bit up-down counter can count from

- a. 000 to 111
- b. 111 to 000
- c. 000 to 111 and also from 111 to 000
- d. none of above

Ans: c

111. A 4 bit down counter can count from

- a. 0000 to 1111
- b. 1111 to 0000
- c. 000 to 111
- d. 111 to 000

Ans: b

112. A mod 4 counter will count

- a. from 0 to 4
- b. from 0 to 3
- c. from any number n to n+4
- d. none of above

Ans: b

113. A counter has modulus of 10. The number of flip flops is

- a. 10
- b. 5
- c. 4
- d. 3

Ans: c

114. The number of flip flops needed for Mod 7 counter are

- a. 7
- b. 5
- c. 3
- d. 1

Ans: c

115. A three-bit up-down binary counter is in the down mode and in the 000 state.

After 3 clock pulses, to what state does the counter go?

- a. 101
- b. 011
- c. 111
- d. 110

Ans: a

116. A three-bit up-down binary counter is in the up mode and in the 110 state.

After 3 clock pulses, to what state does the counter go?

- a. 010
- b. 011
- c. 001
- d. 110

Ans: c

117. A decade counter skips

- a. binary states 1000 to 1111
- b. binary states 0000 to 0011
- c. binary states 1010 to 1111
- d. binary states 1111 and higher

Ans: c

118. Which parts of the computer perform arithmetic calculations?

- a. ALU
- b. Registers
- c. Logic bus
- d. none of above

Ans: a

119. _____ is used to identify particular location in main memory where data is store.

- a. Data Bus
- b. Control Bus
- c. Address Bus
- d. Any other

Ans: c

120. Each box in memory has _____ address.

- a. unique
- b. alterable
- c. two
- d. double

Ans: a

121. Accumulator's main purpose is _____.

- a. temporary data storage
- b. keeping track of the next instruction to be executed
- c. selecting which peripheral should be addressed
- d. storing instructions

Ans: a

122. Microprocessor communicates with the outside world through the _____.

- a. memory
- b. I/O devices
- c. ALU
- d. NONE OF THE ABOVE

Ans: b

123. _____ register gives the address of the memory location from where the next instruction is to be fetched.

- a. Accumulator

- b. SP
- c. PC
- d. any of the above

Ans: c

124. Stack memory is used to_____.

- a. provide additional memory to the base memory
- b. save return addresses of a subroutine
- c. save the status of the microprocessor
- d. none of these

Ans: b

125. _____ includes microprocessor, memory and I/O on a single chip.

- a. microprocessor
- b. microcomputer
- c. microcontroller
- d. none of the above

Ans: c

126. _____ holds the opcode of the instruction.

- a. IR
- b. SP
- c. PC
- d. all of the above

Ans: a

127. _____ holds the address of the top of stack.

- a. IR
- b. SP
- c. PC
- d. all of the above

Ans: b

((MARKS)) (1/2/3...)	2
((QUESTION))	The decimal number equivalent of $(4057.06)_8$ is
((OPTION_A))	2095.75
((OPTION_B))	2095.075
((OPTION_C))	2095.937
((OPTION_D))	2095.0937
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	What is the binary equivalent of the decimal number
((OPTION_A))	101110000
((OPTION_B))	110110000
((OPTION_C))	111010000
((OPTION_D))	111100000
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Determine the values of A, B, C, and D that make the sum term equal to zero.
((OPTION_A))	A = 1, B = 0, C = 0, D = 0
((OPTION_B))	A = 1, B = 0, C = 1, D = 0
((OPTION_C))	A = 0, B = 1, C = 0, D = 0
((OPTION_D))	A = 1, B = 0, C = 1, D = 1
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert 59.7210 to BCD
((OPTION_A))	111011
((OPTION_B))	01011001.01110010
((OPTION_C))	1110.11
((OPTION_D))	0101100101110010
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	Convert $(8B3F)_{16}$ to binary.
((OPTION_A))	35647
((OPTION_B))	011010
((OPTION_C))	1011001111100011
((OPTION_D))	1000101100111111
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Which is typically the longest: bit, byte, nibble, word?
((OPTION_A))	Bit
((OPTION_B))	Byte
((OPTION_C))	Nibble
((OPTION_D))	Word
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert decimal 64 to binary.
((OPTION_A))	01010010
((OPTION_B))	01000000
((OPTION_C))	00110110
((OPTION_D))	01001000
((CORRECT_C HOICE)) (A/B/C/D)	B
((EXPLANATI ON)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert the following octal number to decimal. $(17)_8$
((OPTION_A))	51
((OPTION_B))	82
((OPTION_C))	57
((OPTION_D))	15
((CORRECT_C HOICE)) (A/B/C/D)	D
((EXPLANATI ON)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The sum of $11101 + 10111$ equals _____.

((OPTION_A))	110011
((OPTION_B))	100001
((OPTION_C))	110100
((OPTION_D))	100100
((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Hexadecimal letters A through F are used for decimal equivalent values from:
((OPTION_A))	1 through 6
((OPTION_B))	9 through 14
((OPTION_C))	10 through 15
((OPTION_D))	11 through 17
((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert the following decimal number to hexadecimal. (125)
((OPTION_A))	7D16
((OPTION_B))	D716

((OPTION_C))	7C16
((OPTION_D))	C716
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The binary number 11101011000111010 can be written _____.
((OPTION_A))	DD63A16
((OPTION_B))	1D63A16
((OPTION_C))	1D33A16
((OPTION_D))	1D63116
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	


((MARKS)) (1/2/3...)	2
((QUESTION))	The decimal number equivalent of $(4057.06)_8$ is
((OPTION_A))	2095.75
((OPTION_B))	2095.075
((OPTION_C))	2095.937
((OPTION_D))	2095.0937

((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	What is the binary equivalent of the decimal number
((OPTION_A))	101110000
((OPTION_B))	110110000
((OPTION_C))	111010000
((OPTION_D))	111100000
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Determine the values of A, B, C, and D that make the
((OPTION_A))	A = 1, B = 0, C = 0, D = 0
((OPTION_B))	A = 1, B = 0, C = 1, D = 0
((OPTION_C))	A = 0, B = 1, C = 0, D = 0
((OPTION_D))	A = 1, B = 0, C = 1, D = 1
((CORRECT_CHOICE))	B

(A/B/C/D)	
((EXPLANATION)) (OPTIONAL)	
((MARKS)) (1/2/3...)	2
((QUESTION))	The output of a logic gate is 1 when all its inputs are at logic 0. The gate is either
((OPTION_A))	a NOR or an EX-NOR
((OPTION_B))	an AND or an EX-OR
((OPTION_C))	an OR or an EX-NOR
((OPTION_D))	an NOR or an Ex-OR
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

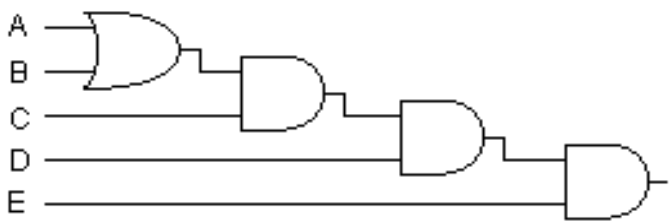((MARKS)) (1/2/3...)	
((QUESTION))	Derive the Boolean expression for the logic circuit 
((OPTION_A))	$C(A+B)DE$
((OPTION_B))	$C(A+B)D+(-E)$
((OPTION_C))	$((C(A+B)D))(-E)$

((OPTION_D))	ABCDE
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)																																									
((QUESTION))	<p>From the truth table below, determine the standard SOP</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th colspan="3">Inputs</th> <th>Output</th> </tr> <tr> <th>A</th> <th>B</th> <th>C</th> <th>X</th> </tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	Inputs			Output	A	B	C	X	0	0	0	0	0	0	1	1	0	1	0	0	0	1	1	1	1	0	0	0	1	0	1	0	1	1	0	1	1	1	1	0
Inputs			Output																																						
A	B	C	X																																						
0	0	0	0																																						
0	0	1	1																																						
0	1	0	0																																						
0	1	1	1																																						
1	0	0	0																																						
1	0	1	0																																						
1	1	0	1																																						
1	1	1	0																																						
((OPTION_A))	$X = \overline{A}\overline{B}\overline{C} + ABC + A\overline{B}C$																																								
((OPTION_B))	$X = ABC + ABC + ABC$																																								
((OPTION_C))	$X = A\overline{B}\overline{C} + \overline{A}BC + A\overline{B}C$																																								
((OPTION_D))	$X = \overline{A}\overline{B}C + \overline{A}BC + A\overline{B}C$																																								
((CORRECT_CHOICE)) (A/B/C/D)	D																																								
((EXPLANATION)) (OPTIONAL)																																									

((MARKS)) (1/2/3...)	2
((QUESTION))	For the SOP expression $A\overline{B}C + \overline{A}BC + A\overline{B}C$, how many 1s are

	in the truth table's output column?
((OPTION_A))	1
((OPTION_B))	2
((OPTION_C))	3
((OPTION_D))	5
((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The 2's complement of the number 1101101 is
((OPTION_A))	0010011
((OPTION_B))	0101110
((OPTION_C))	1101110
((OPTION_D))	1101110
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	A SOP expression is equal to _____
((OPTION_A))	All the variables in domain of expression are present
((OPTION_B))	At least one variable in domain of expression is present.

((OPTION_C))	When one or more product terms in the expression are equal to 0.
((OPTION_D))	When one or more product terms in the expression are equal to 1.
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The expression _____ is an example of _____ tion.
((OPTION_A))	$AB+C = A+BC$
((OPTION_B))	$A(B+C) = B(A+C)$
((OPTION_C))	$AB=BA$
((OPTION_D))	$A+B=B+A$
((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The maximum number that can be represented using unsigned octal system is _____
((OPTION_A))	1
((OPTION_B))	7

((OPTION_C))	9
((OPTION_D))	16
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	2's complement of any binary number can be calculated
((OPTION_A))	adding 1 to 1's complement
((OPTION_B))	adding 1's complement twice
((OPTION_C))	Subtracting 1 from 1's complement.
((OPTION_D))	calculating 1's complement and inverting Most significant bit
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The binary value "1010110" is equivalent to decimal
((OPTION_A))	86
((OPTION_B))	87

((OPTION_C))	88
((OPTION_D))	89
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	
((QUESTION))	A standard POS form has _____ terms that have all the variables in the domain of the expression.
((OPTION_A))	Sum
((OPTION_B))	Product
((OPTION_C))	Min
((OPTION_D))	Composite
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The AND Gate performs a logical _____ function
((OPTION_A))	Addition
((OPTION_B))	Subtraction
((OPTION_C))	Multiplication
((OPTION_D))	Division

((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	NOR gate is formed by connecting _____
((OPTION_A))	OR Gate and then NOT Gate
((OPTION_B))	NOT Gate and then OR Gate
((OPTION_C))	AND Gate and then OR Gate
((OPTION_D))	OR Gate and then AND Gate
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Which of the number is not a representative of
((OPTION_A))	1234
((OPTION_B))	ABCD
((OPTION_C))	1001
((OPTION_D))	DEFH
((CORRECT_CHOICE)) (A/B/C/D)	D

((EXPLANATION)) (OPTIONAL)	
-------------------------------	--

((MARKS)) (1/2/3...)	1
((QUESTION))	The decimal equivalent of the binary number “10011” is
((OPTION_A))	39
((OPTION_B))	99
((OPTION_C))	29
((OPTION_D))	None of given options
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The output of an AND gate is one when _____
((OPTION_A))	All of the inputs are one
((OPTION_B))	Any of the input is one
((OPTION_C))	Any of the input is zero
((OPTION_D))	All the inputs are zero
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The 2s compliment form (Use 6 bit word) of the number 1010 is
((OPTION_A))	111100
((OPTION_B))	110110
((OPTION_C))	110111
((OPTION_D))	1011
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Which of the following expressions is in the sum-of-products (SOP) form?
((OPTION_A))	$(A + B)(C + D)$
((OPTION_B))	$(A)B(CD)$
((OPTION_C))	$AB(CD)$
((OPTION_D))	$AB + CD$
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
-------------------------	---

((QUESTION))	One of De Morgan's theorems states that. Simply stated, this means that logically there is no difference between:
((OPTION_A))	a NOR and an AND gate with inverted inputs
((OPTION_B))	a NAND and an OR gate with inverted inputs
((OPTION_C))	an AND and a NOR gate with inverted inputs
((OPTION_D))	a NOR and a NAND gate with inverted inputs
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The systematic reduction of logic circuits is
((OPTION_A))	using Boolean algebra
((OPTION_B))	symbolic reduction
((OPTION_C))	TTL logic
((OPTION_D))	using a truth table
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The NAND gate output will be low if the two inputs are

((OPTION_A))	00
((OPTION_B))	01
((OPTION_C))	10
((OPTION_D))	11
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The decimal equivalent of hex number 1A53 is
((OPTION_A))	6793
((OPTION_B))	6739
((OPTION_C))	6973
((OPTION_D))	6379
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	$(734)_8 = (?)_{16}$
((OPTION_A))	1DC
((OPTION_B))	1CD

((OPTION_C))	DC1
((OPTION_D))	DCC
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The decimal equivalent of octal number 314 is
((OPTION_A))	210
((OPTION_B))	212
((OPTION_C))	209
((OPTION_D))	204
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	Find out value of X from $(211)_x = (152)_8$
((OPTION_A))	10
((OPTION_B))	7
((OPTION_C))	7.5
((OPTION_D))	16

((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Perform octal subtraction $(161)_8 - (243)_8$
((OPTION_A))	$-(61)_8$
((OPTION_B))	$+(61)_8$
((OPTION_C))	$+(62)_8$
((OPTION_D))	$-(62)_8$
((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Perform Binary Division $(1110101)/(1001)$
((OPTION_A))	$(1101)_2$
((OPTION_B))	$(1011)_2$
((OPTION_C))	$(1110)_2$
((OPTION_D))	$(0101)_2$
((CORRECT_CHOICE)) (A/B/C/D)	C

((EXPLANATION)) (OPTIONAL)	
-------------------------------	--

((MARKS)) (1/2/3...)	2
((QUESTION))	Perform octal multiplication $(14)_8 * (7)_8$
((OPTION_A))	$(124)_8$
((OPTION_B))	$(123)_8$
((OPTION_C))	$(134)_8$
((OPTION_D))	$(213)_8$
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Solve $(105.65825)_{10} = (?)_2$
((OPTION_A))	1101001.10101
((OPTION_B))	1101101.10101
((OPTION_C))	1101100.1101
((OPTION_D))	1011000.0011
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert $(247)_{10} = (?)_8$
((OPTION_A))	366.56
((OPTION_B))	367.54
((OPTION_C))	366.50
((OPTION_D))	366.512
((CORRECT_C HOICE)) (A/B/C/D)	B
((EXPLANATI ON)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert $(32F)_{16} = (?)_{10}$
((OPTION_A))	57.1836
((OPTION_B))	58.1836
((OPTION_C))	57.19
((OPTION_D))	58.177
((CORRECT_C HOICE)) (A/B/C/D)	B
((EXPLANATI ON)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
-------------------------	---

((QUESTION))	Convert $(5826)_{16}=(?)_{10}$
((OPTION_A))	22566
((OPTION_B))	21566
((OPTION_C))	22654
((OPTION_D))	21577
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert $(A72E)_{16}=(?)_8$
((OPTION_A))	123356
((OPTION_B))	123456
((OPTION_C))	213456
((OPTION_D))	123465
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Convert $(4C12E)_{16}=(?)_8$
((OPTION_A))	2312.0456

((OPTION_B))	2313.456
((OPTION_C))	2112.4456
((OPTION_D))	2212.0456
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The output of a logic gate is 1 when all its inputs are at
((OPTION_A))	an NOR or an EX-NOR
((OPTION_B))	an AND or an EX-OR
((OPTION_C))	an OR or an EX-NOR
((OPTION_D))	an NOR or an Ex-OR
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The 2's complement of the number 1101101 is
((OPTION_A))	0010011
((OPTION_B))	0101110
((OPTION_C))	1101110

((OPTION_D))	1101110
((CORRECT_CHOICE)) (A/B/C/D)	A
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	A SOP expression is equal to _____
((OPTION_A))	All the variables in domain of expression are present
((OPTION_B))	At least one variable in domain of expression is present.
((OPTION_C))	When one or more product terms in the expression are equal to 0.
((OPTION_D))	When one or more product terms in the expression are equal to 1.
((CORRECT_CHOICE)) (A/B/C/D)	D
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	The expression _____ is an example of Commutative Law for Multiplication.
((OPTION_A))	$AB+C = A+BC$
((OPTION_B))	$A(B+C) = B(A+C)$
((OPTION_C))	$AB=BA$
((OPTION_D))	$A+B=B+A$

((CORRECT_CHOICE)) (A/B/C/D)	C
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	A group of symbols is known as _____
((OPTION_A))	Boolean expression
((OPTION_B))	Code
((OPTION_C))	Logic expression
((OPTION_D))	Number system
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	In BCD each decimal digit is represented by _____ bit
((OPTION_A))	2
((OPTION_B))	4
((OPTION_C))	6
((OPTION_D))	8
((CORRECT_CHOICE)) (A/B/C/D)	B

((EXPLANATION)) (OPTIONAL)	
-------------------------------	--

((MARKS)) (1/2/3...)	1
((QUESTION))	(1000)Bin is for BCD_____
((OPTION_A))	7
((OPTION_B))	8
((OPTION_C))	9
((OPTION_D))	10
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	From the following which number are valid BCD
((OPTION_A))	1111
((OPTION_B))	1000
((OPTION_C))	1101
((OPTION_D))	All of these
((CORRECT_CHOICE)) (A/B/C/D)	B
((EXPLANATION)) (OPTIONAL)	

((MARKS)) (1/2/3...)	1
((QUESTION))	The largest single digit BCD number is_____
((OPTION_A))	1001
((OPTION_B))	1010
((OPTION_C))	1111
((OPTION_D))	0011
((CORRECT_C HOICE)) (A/B/C/D)	A
((EXPLANATI ON)) (OPTIONAL)	

((MARKS)) (1/2/3...)	2
((QUESTION))	Addition and subtraction of BCD have ____ rules than
((OPTION_A))	Same
((OPTION_B))	Different
((OPTION_C))	--
((OPTION_D))	--
((CORRECT_C HOICE)) (A/B/C/D)	B
((EXPLANATI ON)) (OPTIONAL)	